
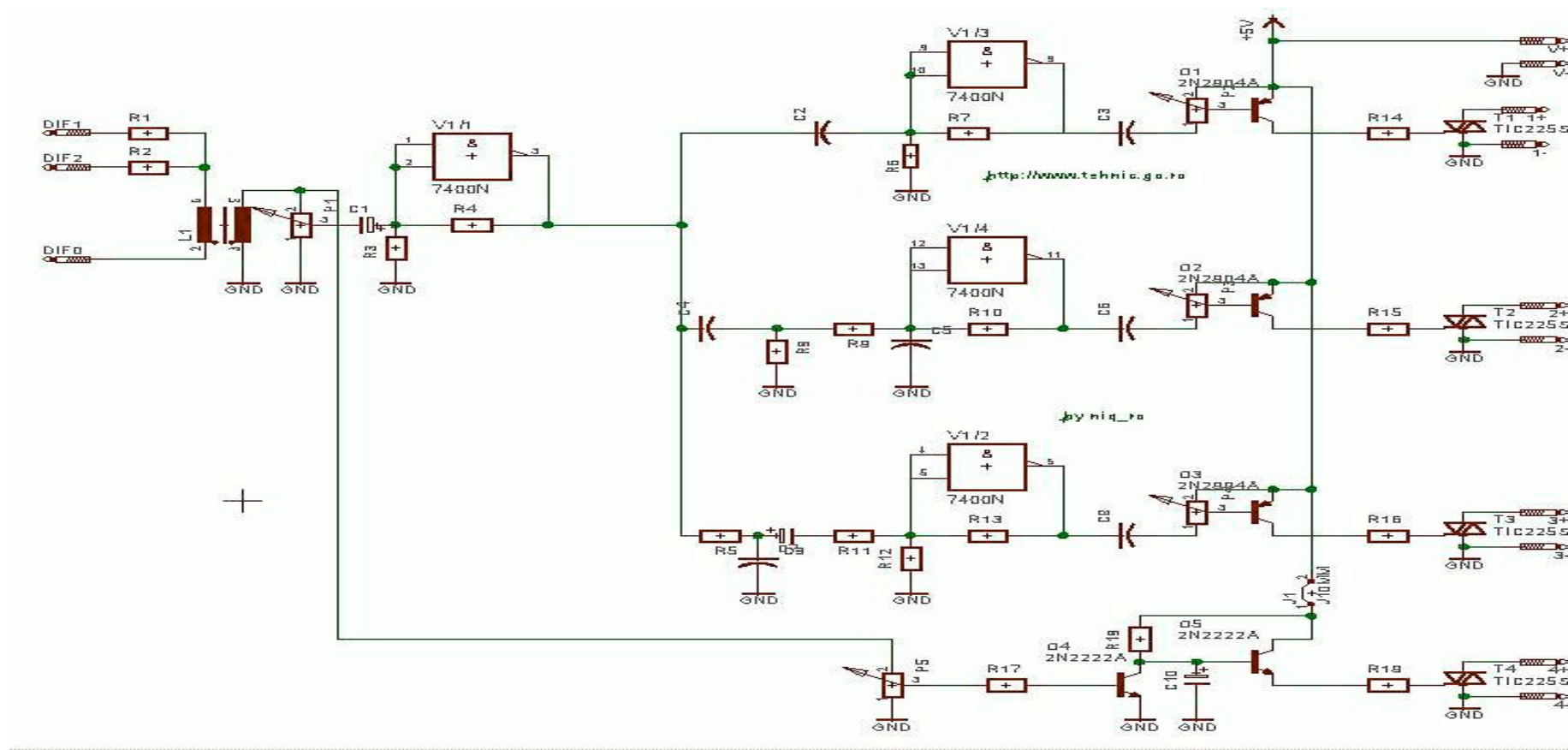


Orga de lumini 3 canale și pauza (negativ)

by niq_ro

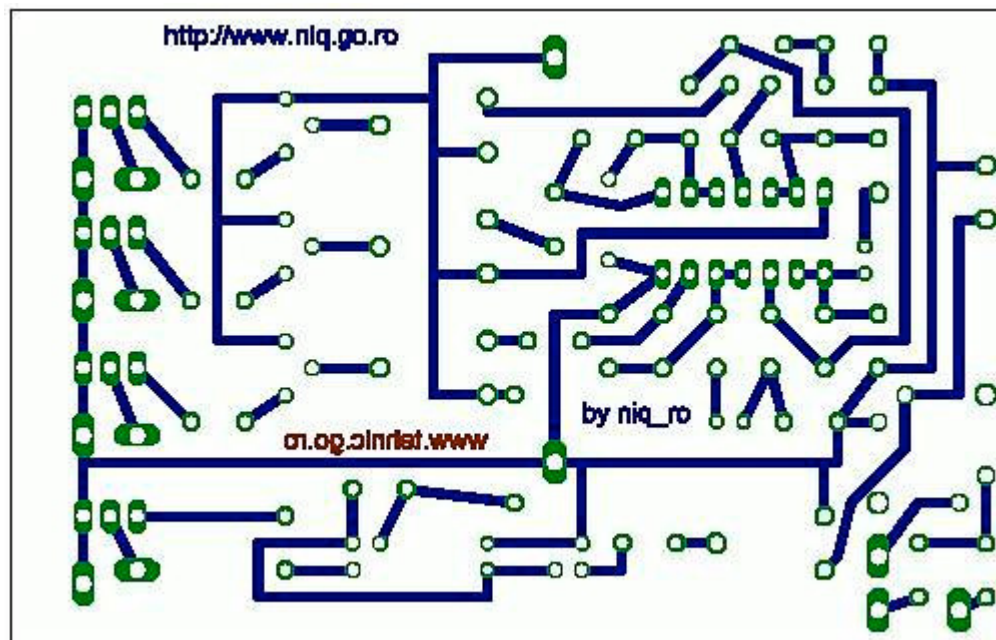



Lista de piese:

R1, R2, R14, R15, R16 - 100Ω

R3, R6, R12 - $2k7$

R4, R7, R10, R13 - $15k$

R5, R8 - $1k5$

R9 - $1k2$

R11 - $1k$

R17, R19 - 470Ω

R18 - $43k$

P1, P2, P3, P4 - $1k$

C1, C8, C10 - $4\mu7$

C2 - $6n8$

C3, C4, C6, C7, C9 - $100n$

C5 - $22n$

Q1, Q2, Q3 - 2N2904, BC177

Q4, Q5 - 2N2222, BC107

V1 - CDB400, 7400 (TTL)

L1 - transformator 1:10 (defazor audio)

Bibliografie:

<http://www.tehnic.go.ro>

revista Tehnium